

Which of the following combine two signals together?

- a) adder
- b) integrator
- c) subtractor